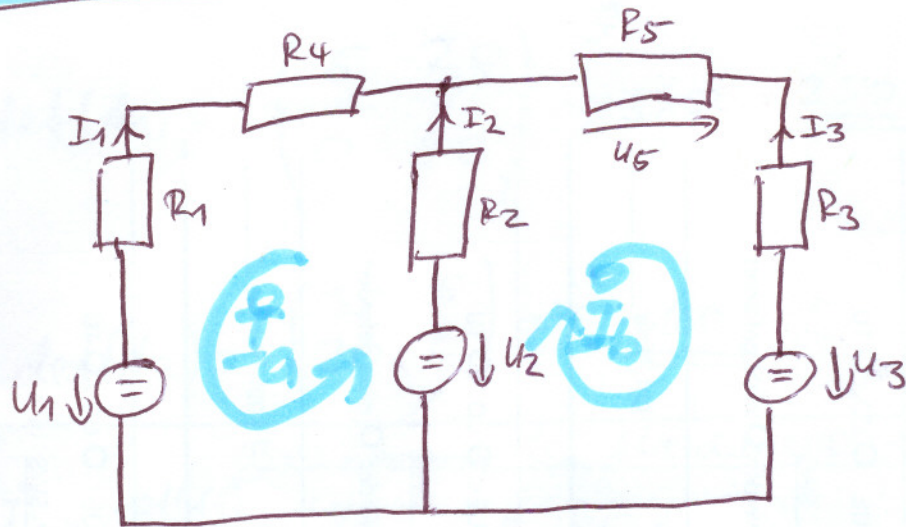


# Übungsblatt 2

## Aufgabe 2:



Werte:  $R_1 = 10\Omega$ ;  $R_2 = 20\Omega$ ;  $R_3 = 20\Omega$ ;  $R_4 = 5\Omega$ ;  $R_5 = 10\Omega$   
 $U_1 = 10V$ ;  $U_2 = 15V$ ;  $U_3 = 15V$

### Meshgleichungen:

$$M1: R_2 \overset{\circ}{I}_a + R_2 \overset{\circ}{I}_b + R_4 \overset{\circ}{I}_a + R_1 \overset{\circ}{I}_a = -U_1 + U_2$$

$$M2: R_2 \overset{\circ}{I}_a + R_2 \overset{\circ}{I}_b + R_5 \overset{\circ}{I}_b + R_3 \overset{\circ}{I}_b = U_2 - U_3$$

### Matrixdarstellung:

$$\begin{pmatrix} R_1 + R_2 + R_4 & R_2 \\ R_2 & R_2 + R_3 + R_5 \end{pmatrix} \begin{pmatrix} \overset{\circ}{I}_a \\ \overset{\circ}{I}_b \end{pmatrix} = \begin{pmatrix} U_2 - U_1 \\ U_2 - U_3 \end{pmatrix}$$

### Konkrete Darstellung:

$$\begin{pmatrix} 35 & 20 \\ 20 & 50 \end{pmatrix} \begin{pmatrix} \overset{\circ}{I}_a \\ \overset{\circ}{I}_b \end{pmatrix} = \begin{pmatrix} 5 \\ 0 \end{pmatrix}$$

$$\det(A) = 35 \times 50 - 20 \times 20 = \underline{\underline{1.350}}$$

$$\det(A_1) = \begin{pmatrix} 5 & 20 \\ 0 & 50 \end{pmatrix} \Rightarrow 5 \times 50 = \underline{\underline{250}}$$

$$\det(A_2) = \begin{pmatrix} 35 & 5 \\ 20 & 0 \end{pmatrix} \Rightarrow \underline{\underline{-100}}$$

Bestimmung der Maschenströme:

$$\dot{I}_a = \frac{\det(A_1)}{\det(A)} = \frac{250}{1.350} = 0,185 A$$

$$\dot{I}_b = \frac{\det(A_2)}{\det(A)} = -\frac{100}{1.350} = -0,074 A$$

gesucht:  $I_1, I_2, I_3$   ~~$I_5$~~

Bestimmung der gesuchten Ströme:

$$\underline{\underline{I_1 = -\dot{I}_a = -0,185 A}}$$

$$\underline{\underline{I_2 = \dot{I}_a + \dot{I}_b = 0,185 A - 0,074 A = 0,111 A}}$$

$$\underline{\underline{I_3 = -\dot{I}_b = 0,074 A}}$$

~~$U_5 = R \cdot I_5$~~   
 ~~$I_5 =$~~



$$\overset{\circ}{I}_a = \frac{\det(A_1)}{\det(A)} = -0,088 \text{ A } (= -88 \mu\text{A})$$

$$\det(A_2) = \begin{pmatrix} 102 & -9 & -1 \\ 1 & -3 & 1 \\ -1 & 6 & 472 \end{pmatrix} = -144429 + 3639 = \overset{-140790}{\underline{\underline{148068}}}$$

$$\overset{\circ}{I}_b = \frac{\det(A_2)}{\det(A)} = \frac{-140790}{13094320} = -0,01075 \text{ A } (= -10,75 \mu\text{A})$$

$$\det(A_3) = \begin{pmatrix} 102 & 1 & -9 \\ 1 & 272 & -3 \\ -1 & 1 & 6 \end{pmatrix}$$

$$= 166458 - 2148 = \underline{\underline{164310}}$$

$$\overset{\circ}{I}_c = \frac{\det(A_3)}{\det(A)} = \frac{164310}{13094320} = 0,012548 \text{ A } (= 12,548 \mu\text{A})$$

$$I_1 = \overset{\circ}{I}_a + \overset{\circ}{I}_b = -88 \mu\text{A} - 10,75 \mu\text{A} = \underline{\underline{-98,75 \mu\text{A}}} \quad \checkmark$$

$$I_2 = -\overset{\circ}{I}_b - \overset{\circ}{I}_c = 10,75 \mu\text{A} - 12,548 \mu\text{A} = \underline{\underline{-1,798 \mu\text{A}}} \quad \checkmark$$

$$I_3 = \overset{\circ}{I}_c - \overset{\circ}{I}_a = 12,548 \mu\text{A} + 88 \mu\text{A} = \underline{\underline{100,548 \mu\text{A}}} \quad \checkmark$$

$$I_6 = \overset{\circ}{I}_a = \underline{\underline{-88 \mu\text{A}}} \quad \checkmark$$